


XO Game

mostafa soliman mohamed fadaly

GORUP:8

this project tell us about
simple game design tic tac
toe this game have played
between two person and
show who will won by using
principles of this game.


logic circuit for game:

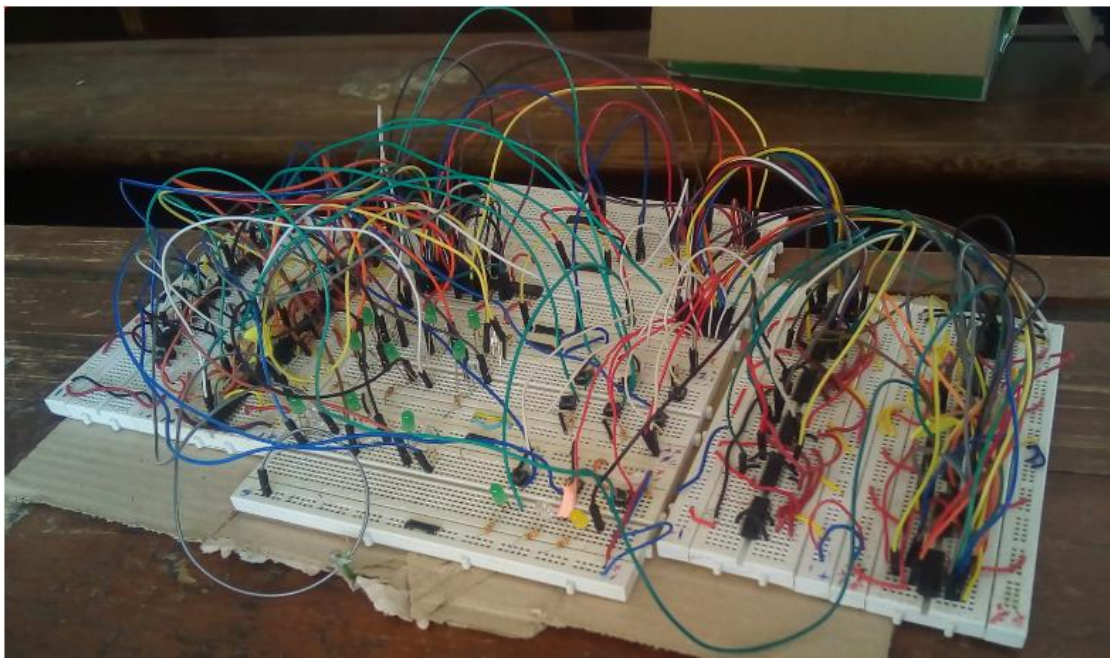

circuit profile player


**I will talk about profile generator
this block diagram which i have
make this with team member
profile generator which shown
below help us to find which
player's turn it's currently it
consists of XOR gate so if no one
has played output will be zero if
number of one is odd output will
be one and if number of one is
even output will be zero.**

logic circuit:-

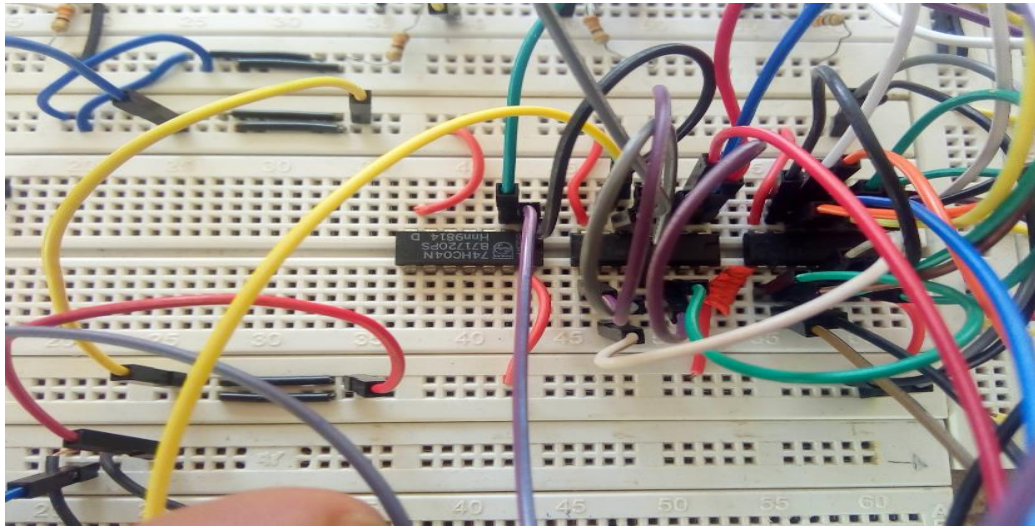


this truth table show this:

INPUT1	INPUT2	OUTPUT
0	0	0
0	1	1
1	0	1
1	1	0

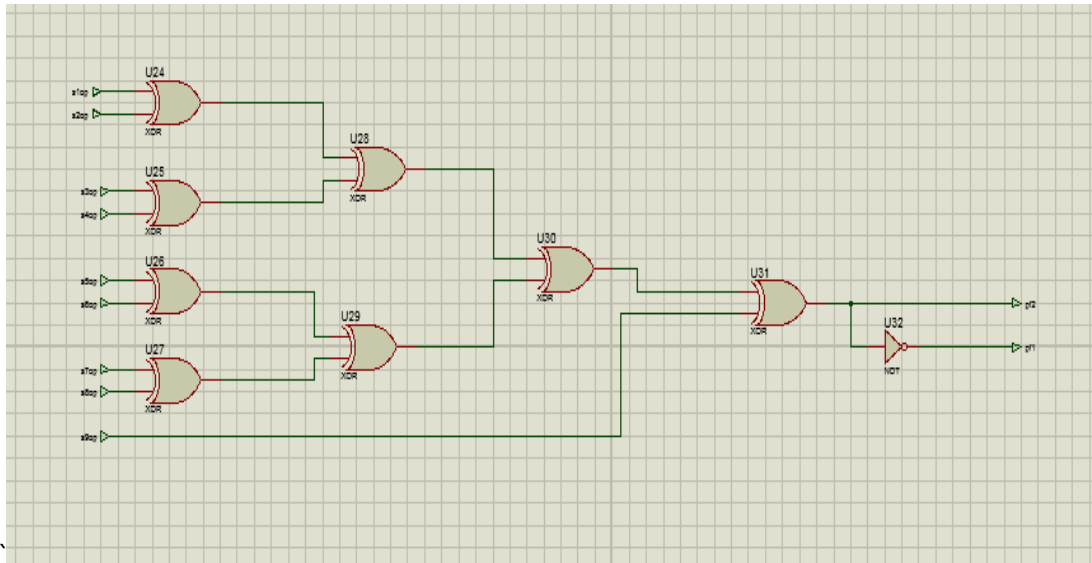

THE INPUT FOR POROFILE:

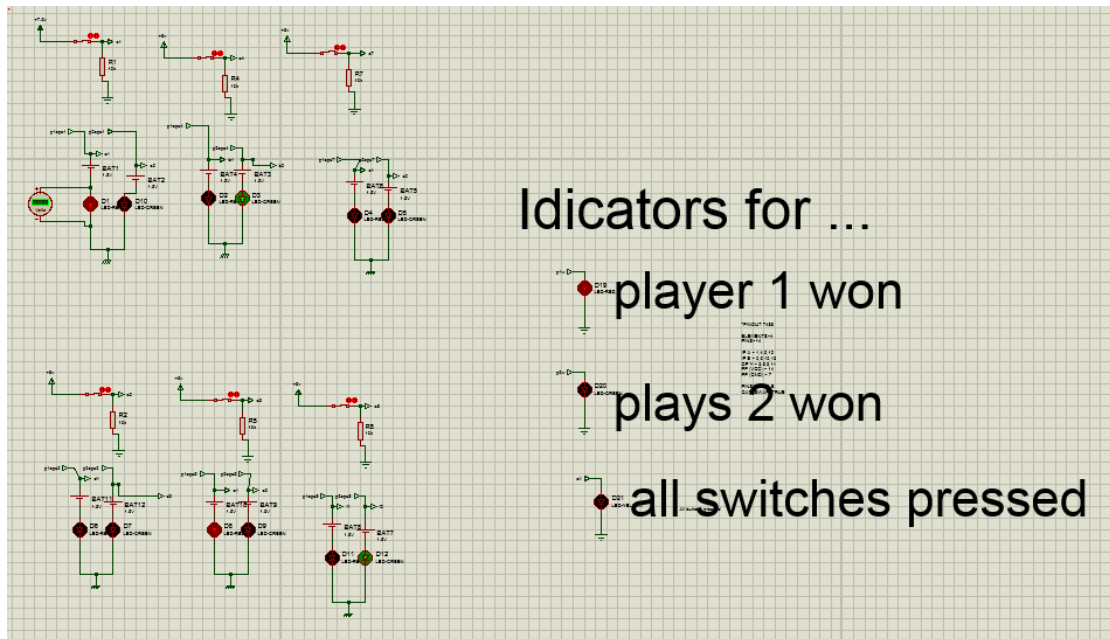

THE OUTPUT FOR POROFIELD:- IS FLEPFLOP

